

## Intro to Robotics

### \* Electric Actuators for Robotics

First Quiz →

Tues 5pm } ED  
Wed 11am } 108  
Fri 8am }

Actuators → elements in a system to create motion - Hydraulic Actuators, Pneumatic Actuators, Electric Actuators.

ESB 208B

Robotics -

• Examples of robots + Drones

Robotic Arm - Pick & Place

Autonomous ability

Assistive devices - Prosthetics

Remotely supervised

Mobile robots - Terrain Mapping

Medicine

Remotely operated system

• Movement

\* Size reasonably small

• Industrial Robots - Pick & Place, Material Handling

• Underwater Robots

Electric

→ \* System should meet operational needs  
↳ → depends on capacity of the actuator

Electronics

→ \* Ability for control

\* Sources for energy

→ industrial robots stationary (welding robots)

Electric actuation is preferred.

underwater robots

Battery / Long cable.

→ Remotely Operated Armoured Vehicle

Diesel engine → generate electricity

↓


Actuators → we need high torque but low weight of the actuator. Therefore we mainly consider "torque / weight" ratio for performance

Hydraulic is best, but very hard maintenance and so we are moving away. The next best is Electric Actuator

### Electric Actuators - Motor | valves

DC or AC

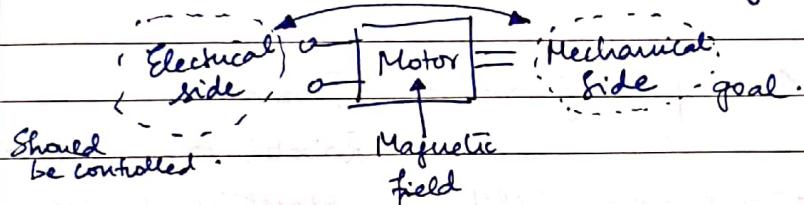Motors → Electro-Mechanical energy conversion



DC motors

AC motors

- Induction motor
- Synchronous motor


Brushless DC motor

Permanent Magnet Synchronous motor


### Variable Reluctance

- Stepper Motors
- Switched Reluctance Motors
- Synchronous Reluctance Motors

Operational Need → Torque capability

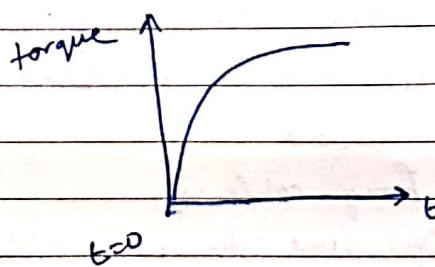


Actuator -1

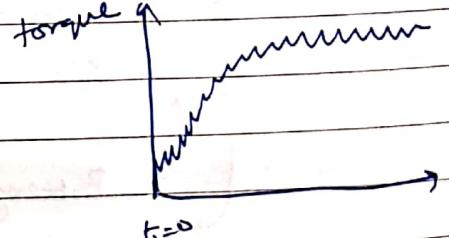

Actuator -2

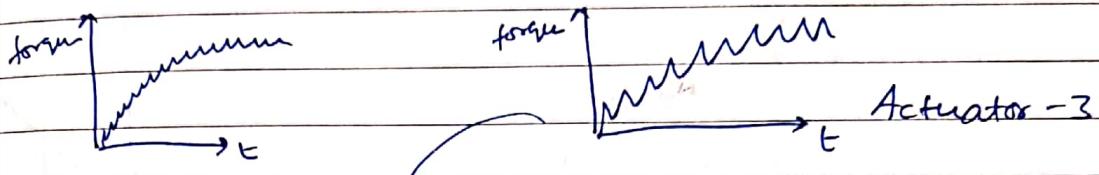Although the torque oscillates in actuator-2, doesn't necessarily mean the <sup>robot</sup> body vibrates. Vibration depends on more factors like moment of inertia and damping. Although the actuator vibrates, the body doesn't necessarily.



this has lower frequency,  
& more amplitudes.


Mechanical systems have very low resonant frequency. In that case, higher frequency is better as the second case might match the resonant frequency and lead to vibration.

$\therefore$  It is alright to have Act-2, as long as it falls in system allowance.

### Speed of movement

motor speed vs load speed

21<sup>st</sup> Jan, 2020

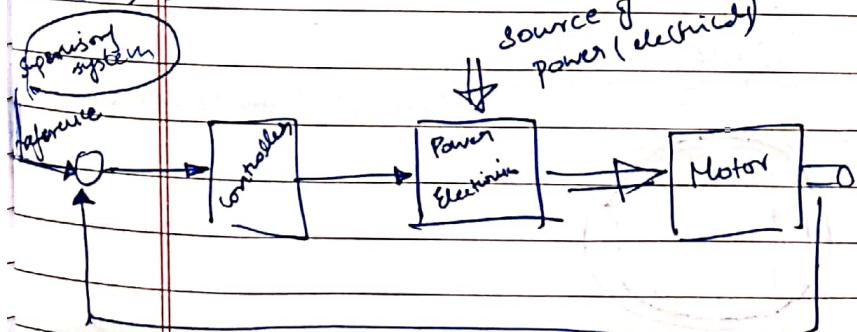

### Books:

1. Modern Power Electronics

& AC Drives

(B. K. Bose)



2. DC drives

(R. Krishnam)

## Electric Motors

\* DC Motors  $\rightarrow$  2 basic structural parts  
(rotating)


motor      stator

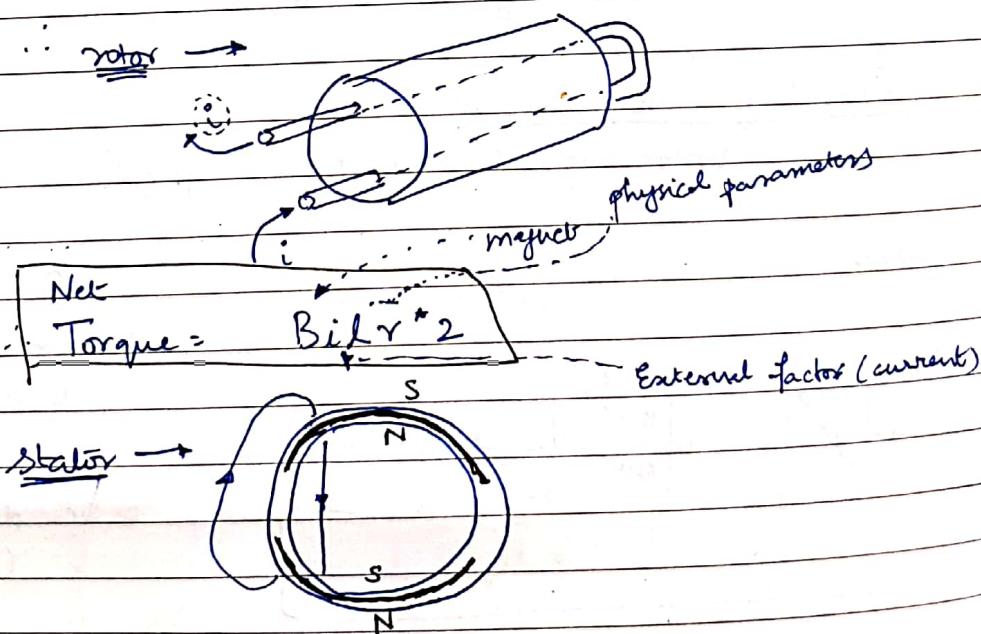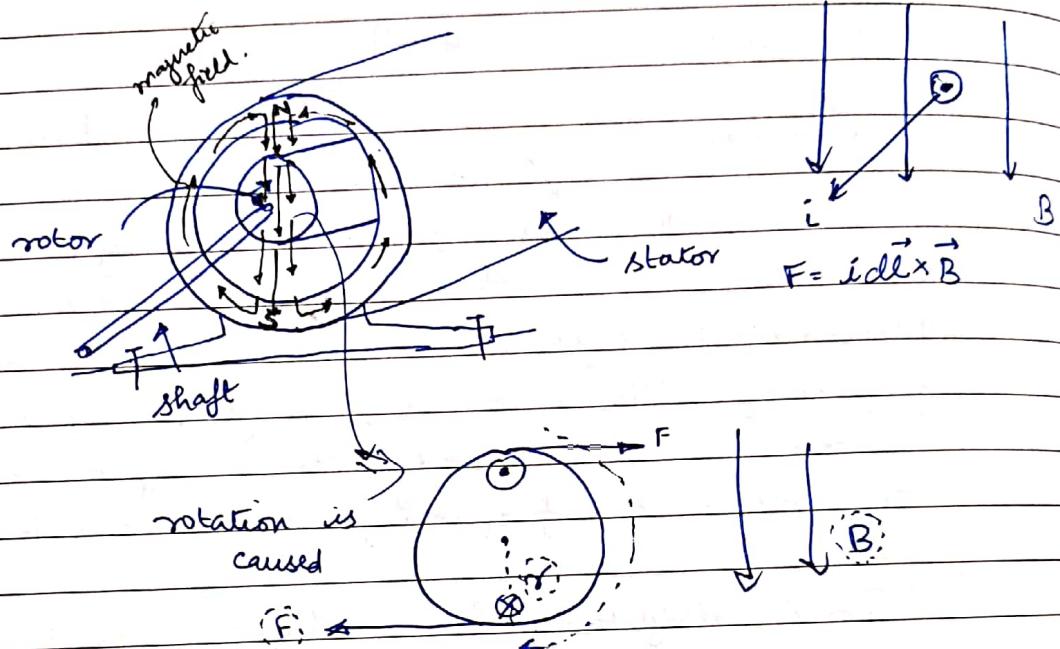

\* Faraday's law :

$$\text{emf} = Blr \cdot 2\omega$$

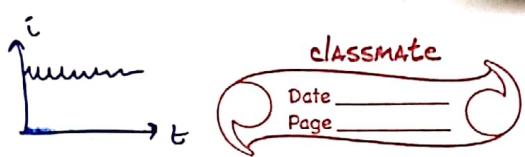This is allowed if magnitude of ripple is small enough frequency is high enough.



Therefore for a motor.

$$\begin{aligned} \text{Torque} &= k_i \\ \text{Emf} &= k_w \end{aligned} \quad \left. \begin{array}{l} \text{Torque} = k_i \\ \text{Emf} = k_w \end{array} \right\} k = 2 Blr$$


\*Lenz's law : Induced EMF will attempt to resist change in flux.

Equation :

$$V = IR + k_w \quad T = k_i$$

→ applied voltage  
→ inertia, opposing forces.


for a pure DC motor,

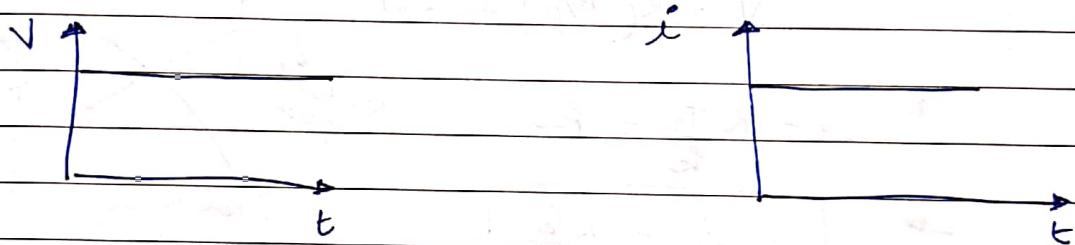

The input current, being a constant is better as it affects the torque proportionally. and so will there be a constant output torque and motion. Meanwhile constant V is not mandatory.

22/11/2020 Stator  $\rightarrow$  Field Assembly  $\rightarrow$  magnets

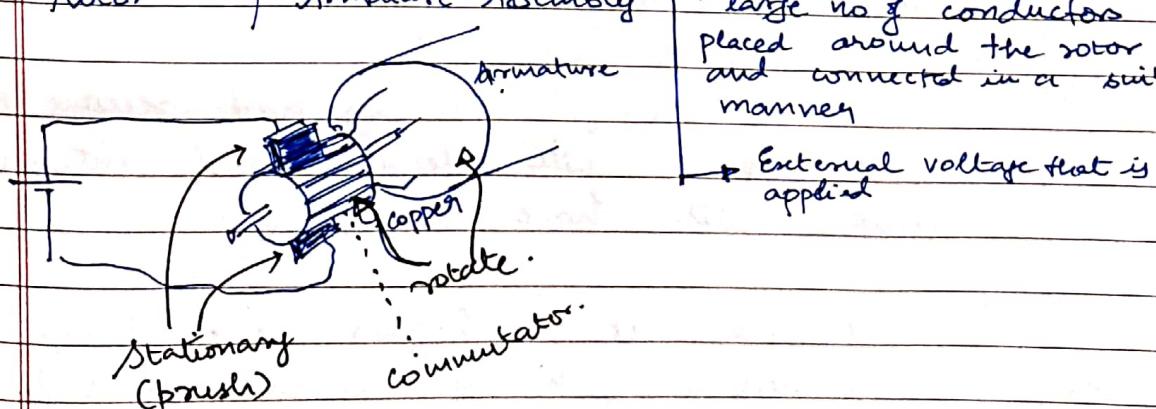Rotor  $\rightarrow$  Armature Assembly  $\rightarrow$  large no of conductors placed around the rotor and connected in a suitable manner



$$V = IR + k\omega \quad | \quad \text{Steady state equation.}$$

$$V = iR + L \frac{di}{dt} + k\omega \quad ? \quad \text{Motor equations.}$$

$$T_e = k_i i$$

$$J \frac{dw}{dt} = k_i i - T_L \quad \rightarrow \text{external load torque}$$

(e.g.: Robotic hand lifting an object experiences torques)

$$= k_i i - B\omega - T_{L0} - T_L$$

### \* Torque Vs Speed


$$V = ER + iR + k\omega$$

$$V = R(T_e/k) + k\omega$$


$$\Rightarrow V - R \frac{T_e}{k} = k\omega$$

$$\Rightarrow \boxed{\omega = \frac{V}{k} - \frac{R T_e}{k^2}}$$

$$y: V/k \quad \text{slope: } -R/k^2$$

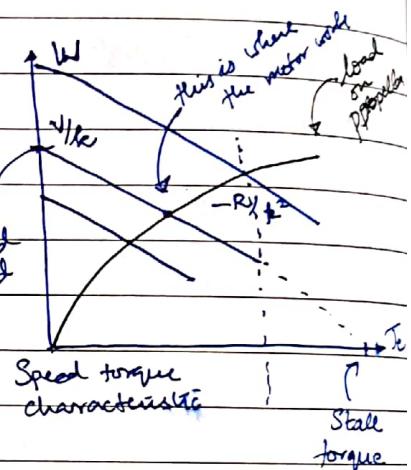

(Tmax)

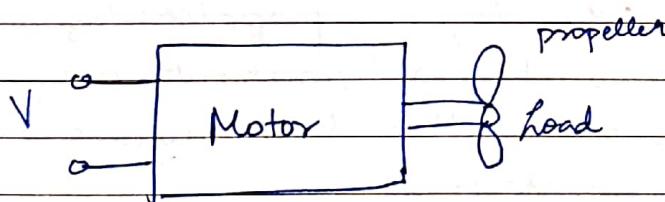


### Underwater Mobile Robotic Application:

Now, to have the motor intersect the load graph at a different ' $\omega$ ', the resistance outside could be changed. We can add resistor outside, the slope will decrease and intersecting point will have lower ' $\omega$ '.

To intersect at a higher ' $\omega$ ', change  $V$ , intersection with y-axis will go higher, thereby no intersection happens at a higher ' $\omega$ '.



Rating of the motor : Max Voltage  
 Max Current  
 Max Speed

\* Armature Voltage Control desirable

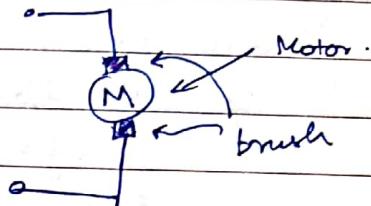

\* We can add resistor to give the motor a specific voltage, but resistor eat up power supplied.

24/1/2020 Permanent Magnet

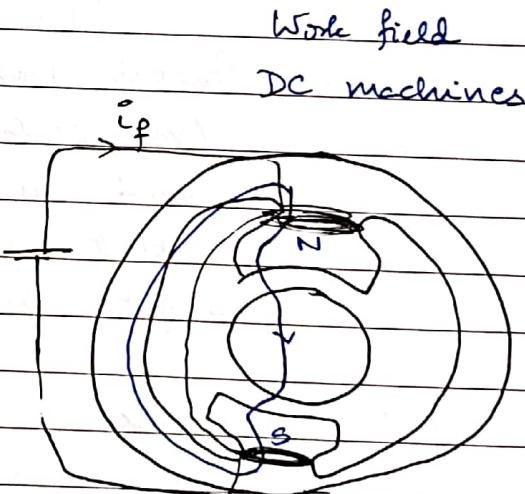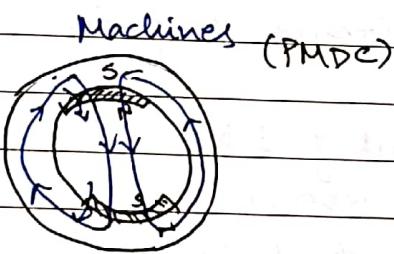

In the case of WFDc, we can change the magnetic field as well.

(Bigger)

Max Voltage  $\propto e \propto Bw$

Generated Electromagnetic Torque  $\propto B_i$

Generated EMF  $\propto Bw$

Rating :

$$\text{Max. Speed} = 100 \text{ rad/s}$$

$$i = 5A$$

$$\text{Max. Torque} = 5 \text{ Nm}$$

$$B = 1 \text{ Wb/m}^2$$

If I need 4 Nm torque, I can choose

$$B = 2 \text{ Wb/m}^2 \quad i = 2$$

$$B = 0.5 \quad i = 8$$

$$B = 0.25 \quad i = 16$$

∴ When we can change, we choose  $B_d$  such that 'B' is taken to be the max rating and corresponding  $i$  for the case.

$$B = B_{\text{max}} \quad (\text{send correspondingly } i)$$

→  $i_{\text{min}}$  for a required torque taken

Incase we need to go to higher speed than rated.

Eg. 300 rad/s.

$\text{Emf} = Bw$  and the machine cannot handle more Emf as the machine cannot handle the same. So, we reduce 'B' for according new 'w'. and keep the Emf controlled.

Electrical power input to machine:

$$\sqrt{i} \leftarrow \text{limited by machine rating}$$

Output power : Torque  $\times$  Speed.

(mechanical)

if we need an output of 5 Nm at higher speed,

$$\text{output power} = 1500 \text{ W}$$


but input power is fixed ( $V_{\text{max}} \times i_{\text{max}}$ ) = 500 W

(300)



$\frac{\text{rated}}{\text{rated}}$

∴ To increase

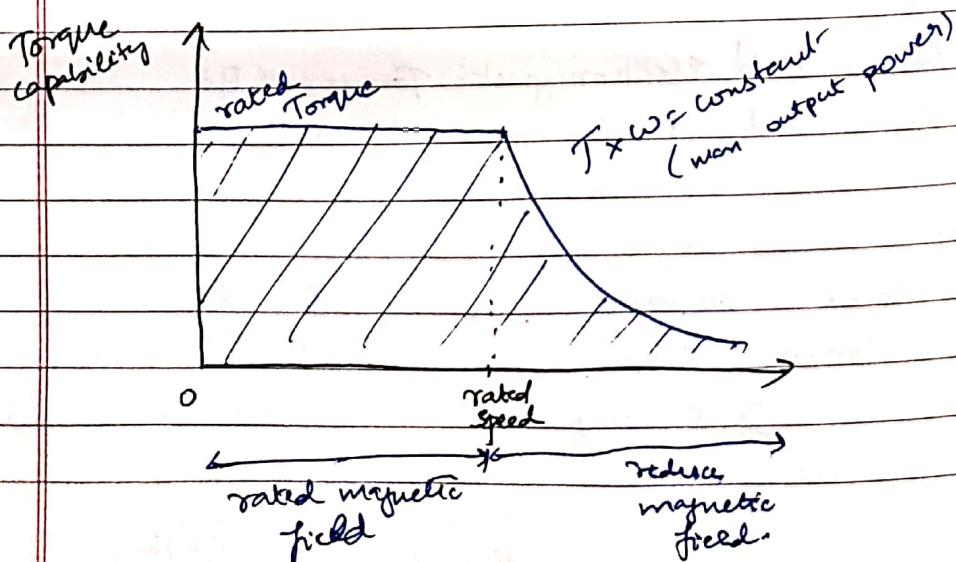Field weakening: More torque that can be allowed mode to be generated reduces with speed.





## \* Power Electronics:

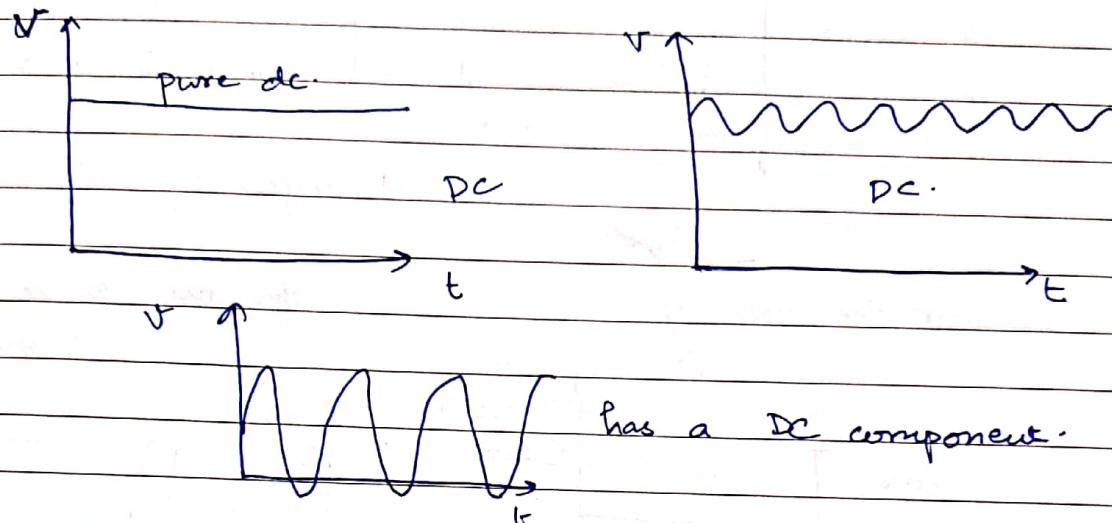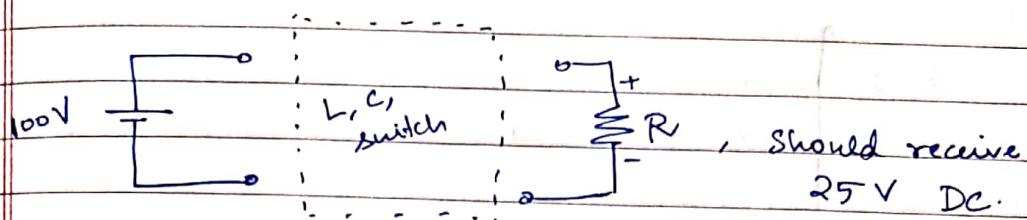


dc = waveform with non-zero dc component.

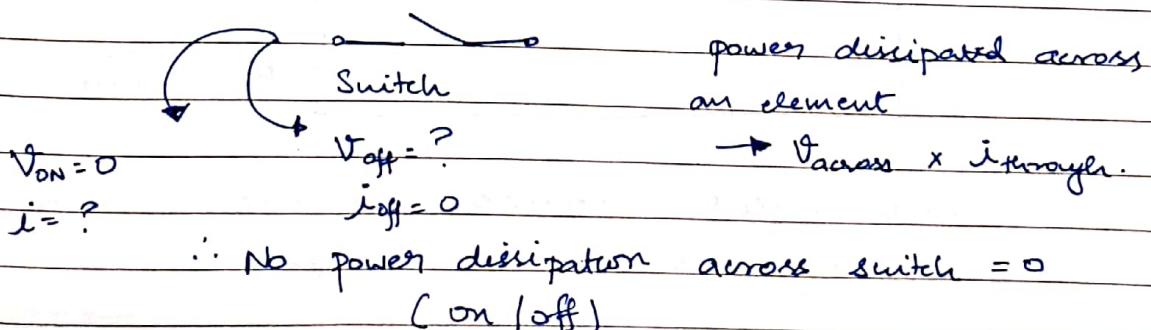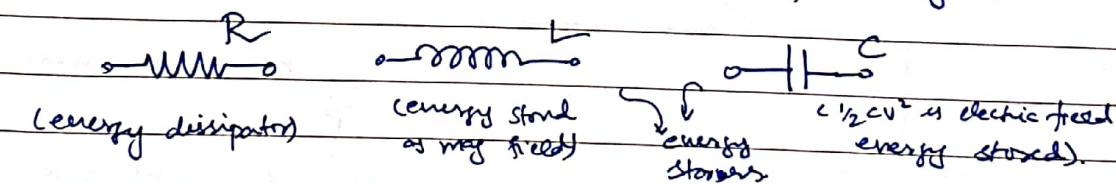A resistor only dissipates electric power, irrespective of nature of input voltage. To give ~~pure DC component~~ to an output, we use the following.




So, to give a DC component, we can use switch, inductor + capacitor.

to give a DC component of 25V,

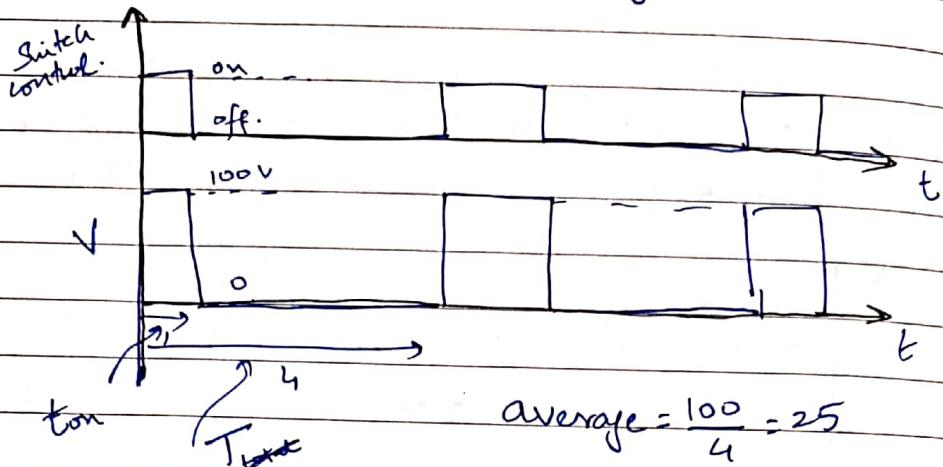

For the case of

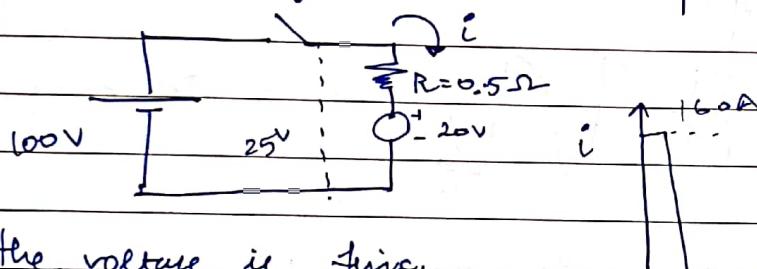


for the same switch controls

the voltage is fixed

but for a current flow with above wave form  
won't be suitable for the motor. As em torque  
generated is a function of instantaneous  
current.

28<sup>th</sup> Jan 2020

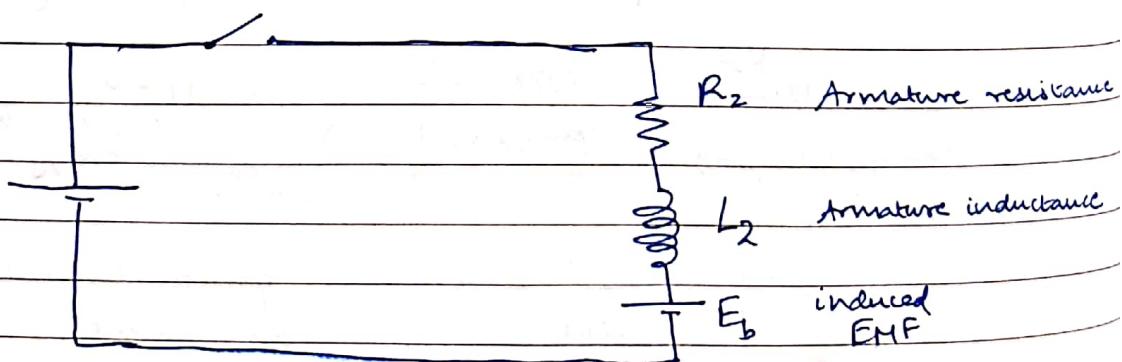


We'll neglect armature resistance as we're only considering the dynamics analysis now.

in case we had a switch, and we closed  
the switch for analysis

$$V_g - \frac{L_a}{I} E_b = L_a \frac{di}{dt}$$
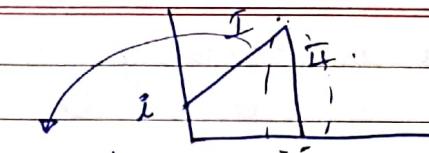
$$\Rightarrow \frac{di}{dt} = \frac{V_g - E_b}{L_a}$$




then if we turn

the switch off, the current becomes 0

& then the saved energy will be dissipated as heat and would cause huge fire across switch.

Now we had a diode,

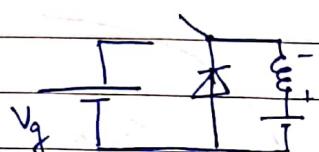


this diode will not charge during first phase and acts as a wire in the second phase.


$\therefore$  The graph becomes better

$$L_a \frac{di}{dt} = 0 - E_b$$
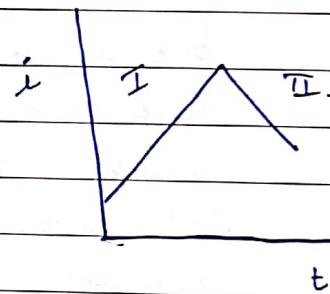
$$\therefore \frac{di}{dt} = -\frac{E_b}{L_a}$$



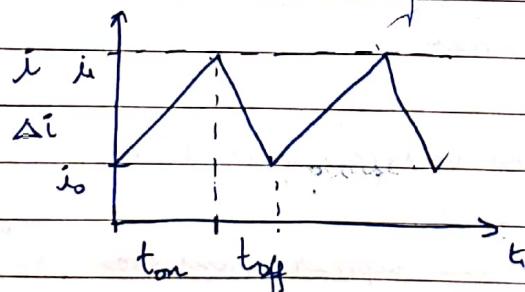Continuing with sequential ON & OFFs,  
we obtain



Here, the magnitude and frequency of the ripple is in control

$$\Delta i = \left( \frac{V_g - E_b}{L_a} \right) t_{0n}$$

$\Rightarrow$  for a given  $E_b$  ( $\Rightarrow \omega$ )

smaller magnitude of ripple =

$$= \left| -\frac{E_b}{L_a} \cdot t_{0ff} \right|$$

We can reduce  $t_{0n}$  but reducing it too much would result in less avg voltage supplied (check) (V vs t graph in previous page). So T has to be reduced as well.

$\therefore$  conclusion  $\rightarrow$  decrease  $t_{0n}$

decrease  $T_{0ff}$

switching frequency made higher.

It is necessary to use switching circuits.  
Switches cannot be mechanical.

⇒ use electronic switch

Preferable to have higher switching frequency.  
(10,000 Hz to 20,000 Hz)

→ Low ripple current

⇒ Estimate value

actual:

$$R_i + L_a \frac{di}{dt} = V_g - E_b \Rightarrow$$

(first order)

$$\text{Time constant} = \frac{L_a}{R_i}$$

but usually, cases have high time constant and we will be switching off much sooner. This makes the initial fall look linear and this supports our initial assumption and matches the calculation (prev page)

Electronics used:

\* MOSFET ← n-channel  
p-channel

Enhancement mode

Depletion mode

commonly used as the switch

Fully  
Controllable  
Device

→ used in low voltage applications


\* IGBT - Insulate Gate Bipolar Transistor

(high voltage  
application)


Uncontrollable  
device

\* Diode - Circuit conditions decide the working.

MOSFET

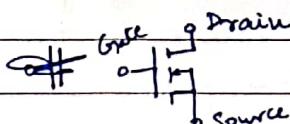


IGBT

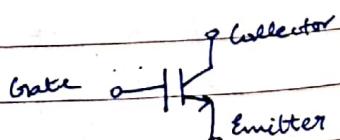

FET: Applying a suitable voltage across Gate - Source  
IGBT: Voltage across Gate - emitter

In a circuit,

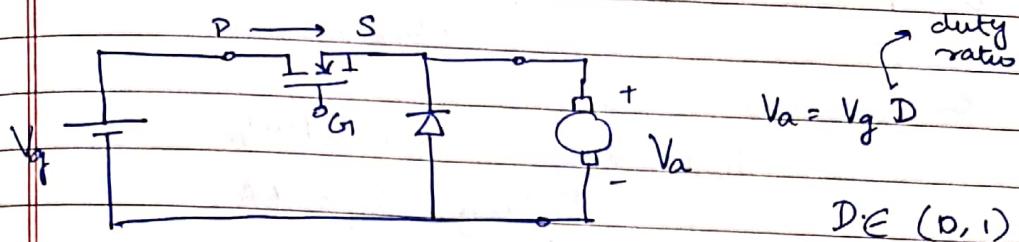


Switching circuits need freewheeling diodes..

\* Reverse a Motor :

Apply reverse voltage  
A 'D' cannot go other than (0-1),  
the circuit above will not be able to  
run the motor in reverse.

∴ Modified circuit :

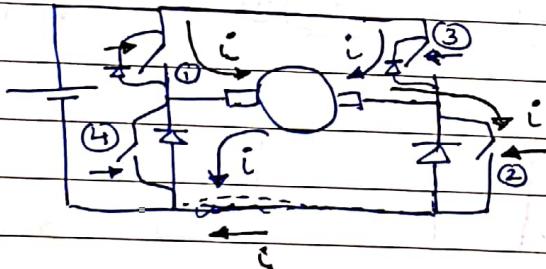

turn on ① & ②

for mode of  
operation as seen  
earlier.


turn on ③ & ④

for motor to run  
in the opposite direction.

The above circuit is a H-bridge configuration  
tve, -ve : by that we mean the average voltage  
across the motor, and not the instantaneous  
voltage.

29/11/2020

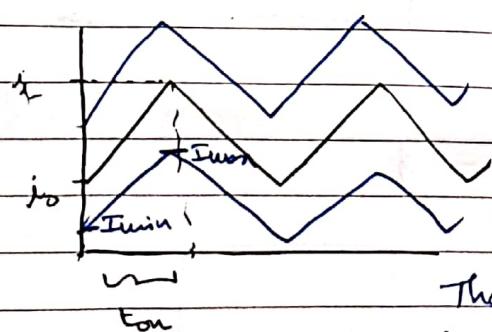All those,  
same  
ripple  
characteristics



$$\Delta i = \frac{V_g - E_b}{L_a} \cdot t_{on}$$

$$\Delta i = \left( -\frac{E_b}{L_a} \cdot t_{off} \right)$$

These equations only talk about  
the ripple magnitude and frequency  
and does not specify anything about the  
avg. current .

DC Motor :  $T_e = T_{load} = kI$  the average current  
load on motor

for instance




$$\text{if } T_{load} = 6 \text{ Nm} \quad k = 1 \text{ Nm/A}$$

$$\Rightarrow I_{avg} = \frac{k}{1} = 6 \text{ A}$$

Equations to be used :

$$\left. \begin{array}{l} I_{max} - I_{min} = \Delta i \\ I_{max} + I_{min} = I_{avg} \end{array} \right\} \frac{I_{max} - I_{min}}{2}$$

for the circuit,

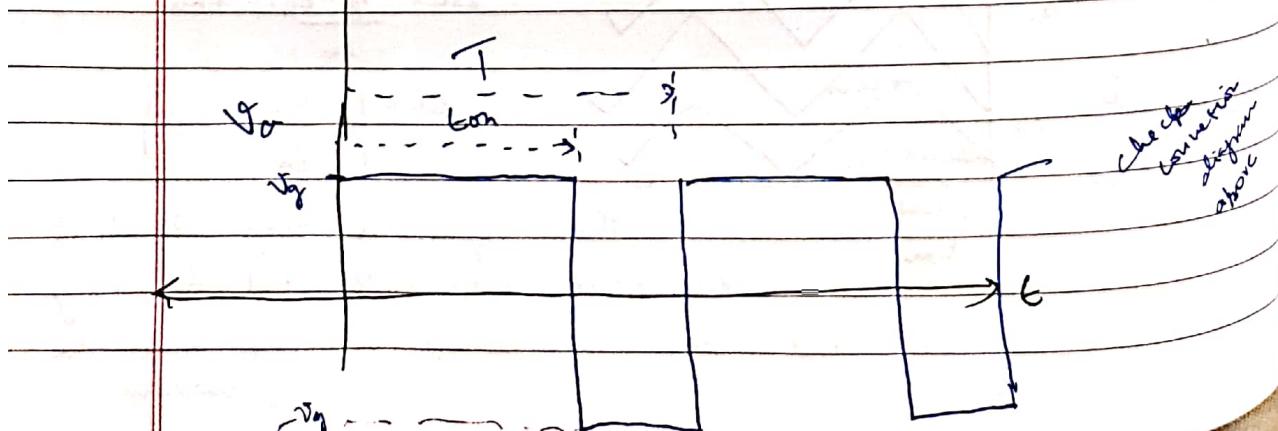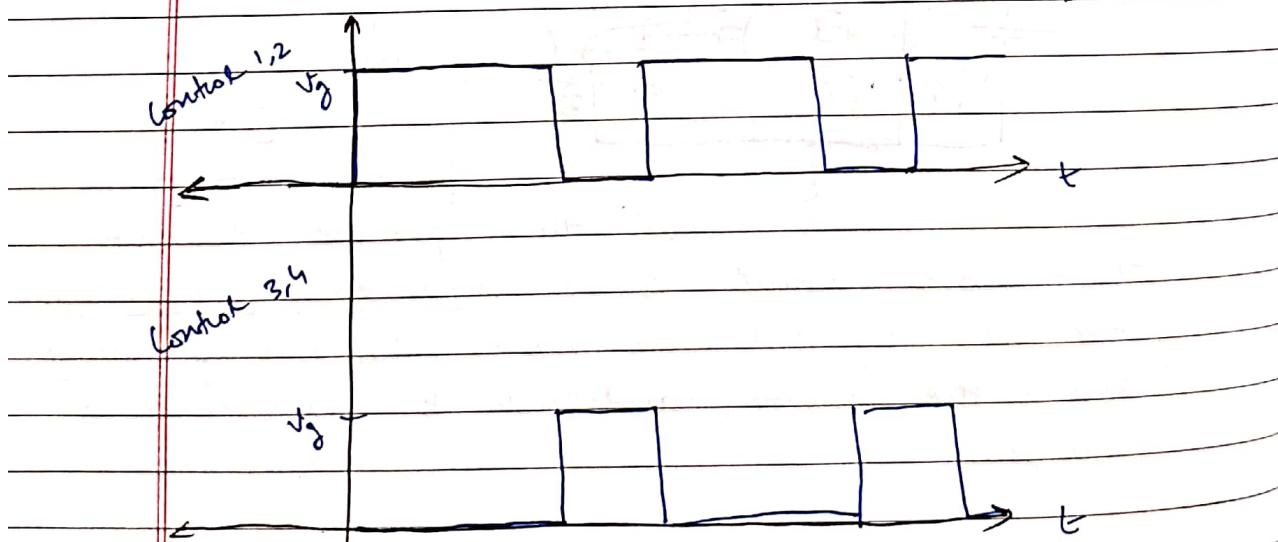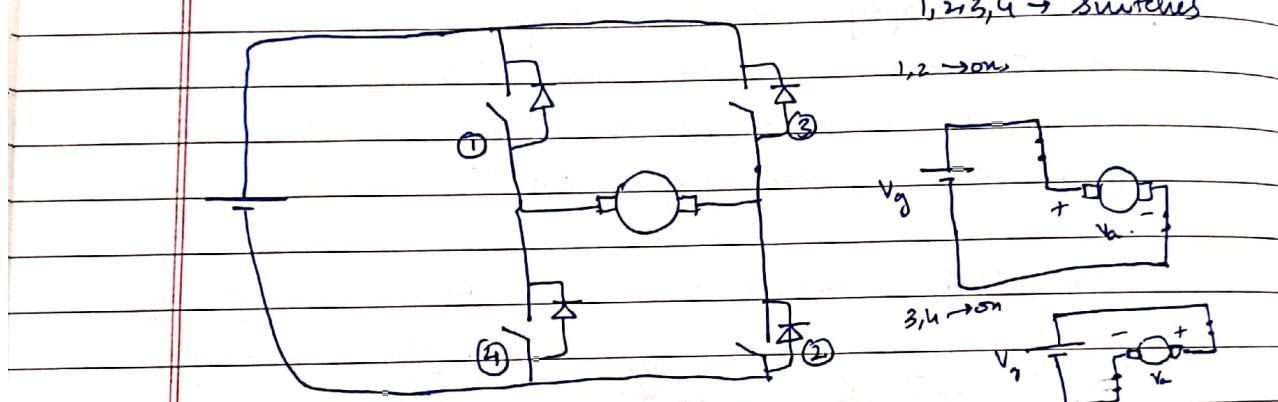

$$\therefore V_a = \frac{V_g t_{on} - V_{loff}}{T} = \frac{V_g t_{on} - V_g (T-t_{on})}{T}$$

$$= \frac{2 V_g t_{on} - V_g T}{T} = V_g \left( \frac{2D-1}{T} \right)$$

duty ratio  $D = \frac{t_{on}}{T}$


$\therefore$  Now for this case, if  $V_a > 0$ ,  
then the setting must be  $D > 0.5$

$$V_a > 0 \mid D > 0.5$$

$$V_a = 0 \mid D = 0.5$$


$$V_a < 0 \mid D < 0.5$$

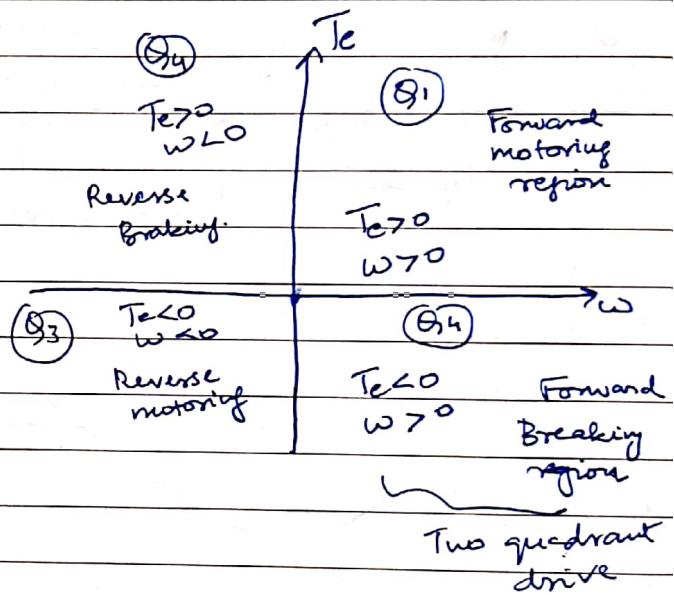Let us consider  
the case of a  
robotic arm




a

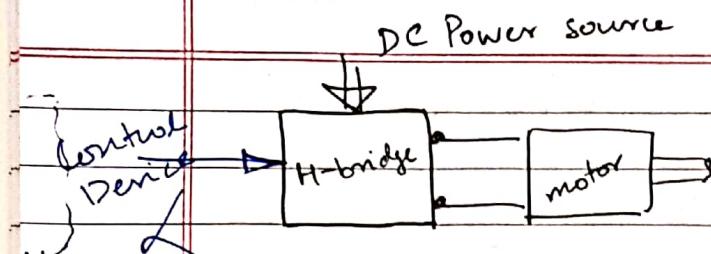A circuit that  
allows a motor  
to operate in  
all 4 quadrants  
above is a  
4-quadrant drive.  
Eg: H-bridge.



→ Should give instructions on when switches should be triggered

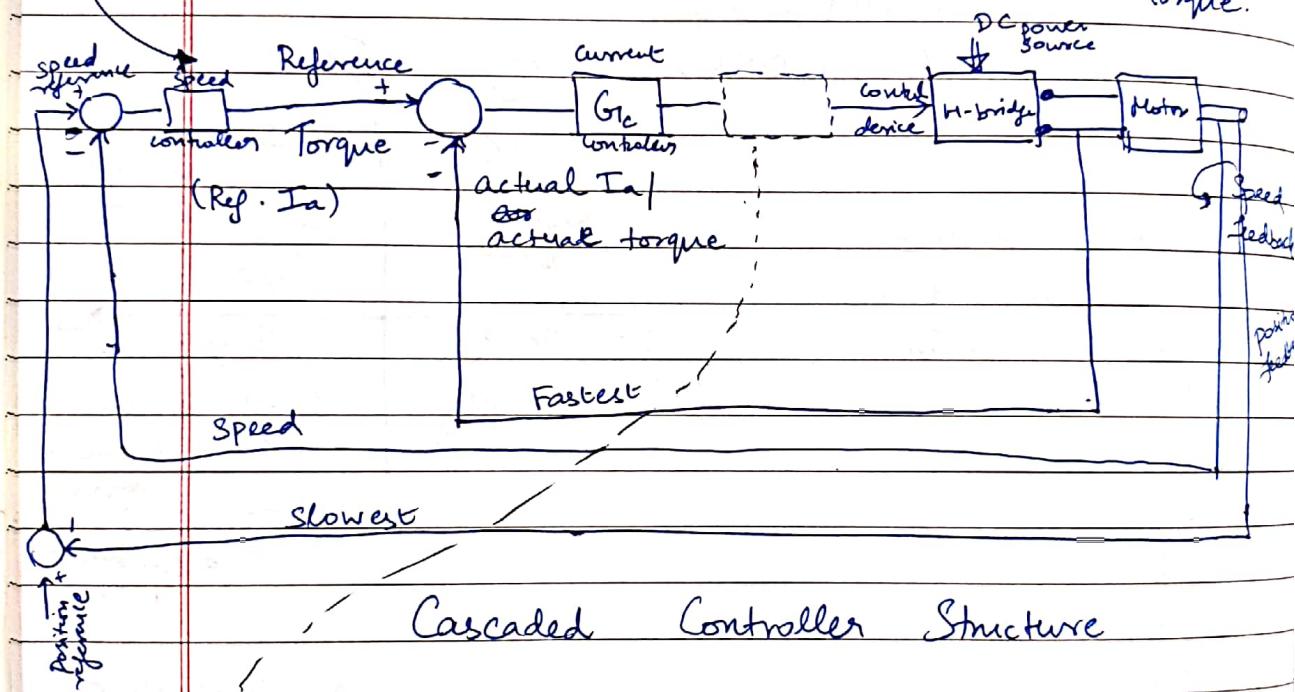The electrical subsystem of the motor is the first thing that responds first  
→ responsible to generate electromagnetic torque.




### Cascaded Controller Structure


→ The output of  $G_c$  → analog voltage  
→ number

The input H-bridge requires → Switching controls  
This conversion is done by 'Modulator'.

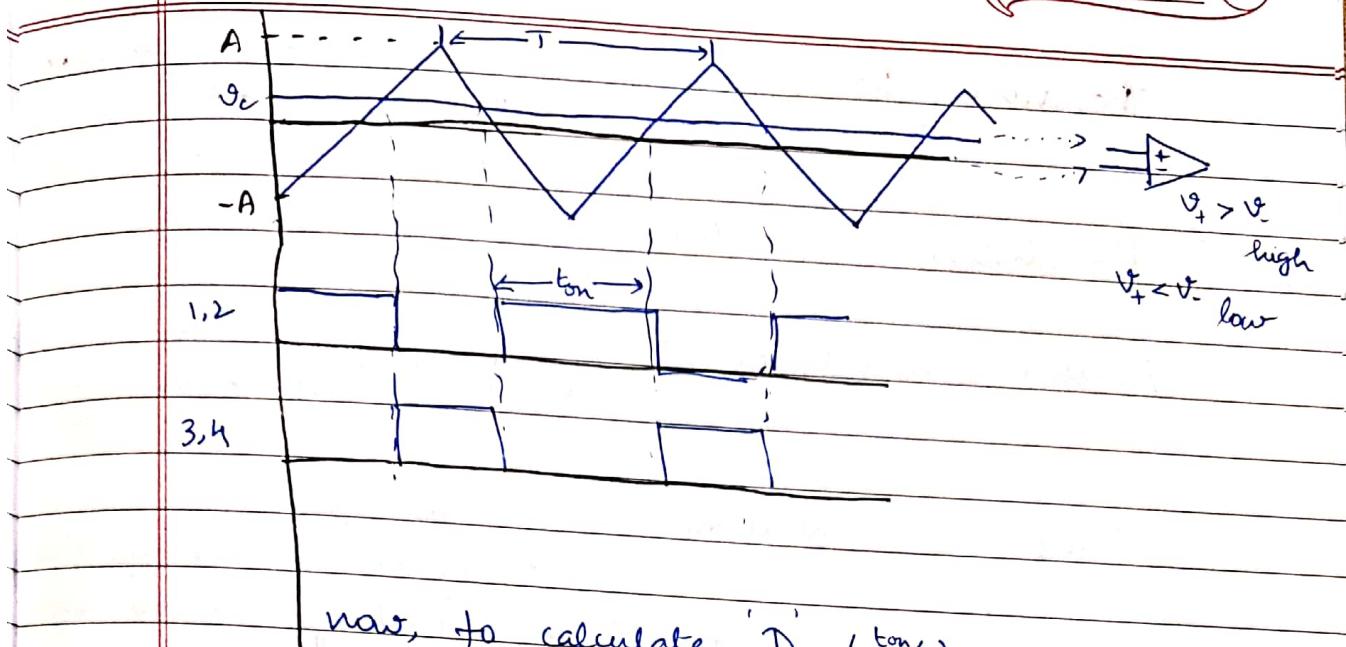★ Earlier we saw, the  $T_m$  to  $T$  can be changed to alter the average  $V$ . So theoretically, we modify the pulse width. So the term "Pulse width Modulation".



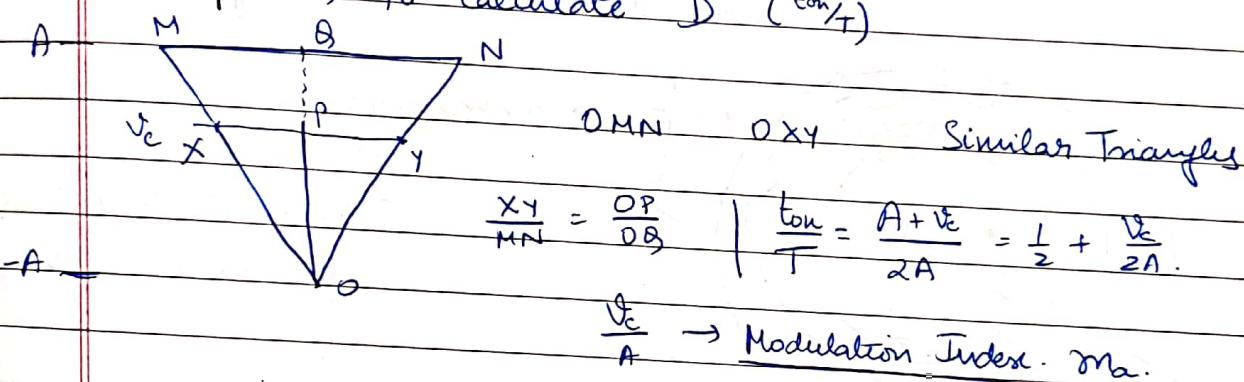now, to calculate 'D' ( $\frac{ton}{T}$ )




$$V_a = V_g \left[ \frac{2(m_a + 1)}{2} - 1 \right] \quad D = \frac{1}{2} + \frac{m_a}{2} \quad m_a/2$$

$$V_a = V_g \left[ \frac{2(m_a + 1)}{2} - 1 \right] = m_a V_g \quad = \frac{m_a + 1}{2}$$

DC Motor Control Structure:

field generated at stator.

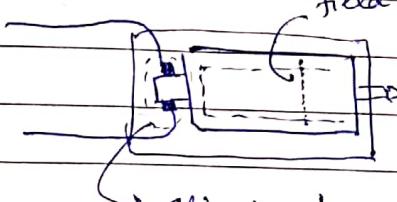

→ Slipping brushes: requires to tackle sliding friction.

∴ Brushes are made of Graphite.

Graphite → soft. With use, the brushes erode. Eroded material settles on the cylinder, shorts between input & output.

∴ DC Motors are not used in Robotic Applications.

The next best alternative is a BLDC machine  
(brushless DC)


3/11/2020

## Brushless DC Motors


Brush + commutator  $\Rightarrow$  stationary power source  
→ they have to energize the rotating member

Brushless  $\Rightarrow$  stationary power source


then, the field should go on the rotor

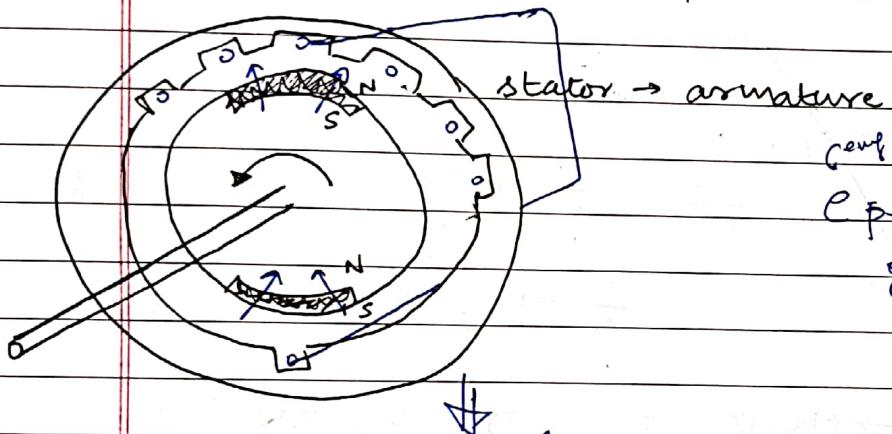

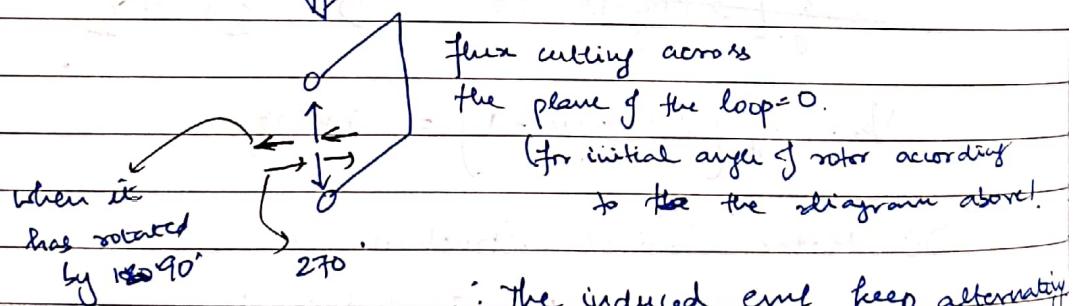$E \propto \text{rate of change of flux}$



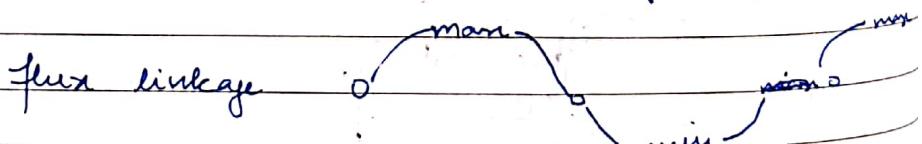$\therefore$  The induced emf keeps alternating



$e \rightarrow \text{alternating}$

$\Rightarrow$  cannot connect a DC source to this


$\therefore e = \text{AC waveform}$

$\hookrightarrow$  frequency depends on speed amplitude also depends on speed.

∴ An AC source where magnitude & frequency can be controlled should be synchronous with the 'e'.

### 3-phase machines

(3 groups = phases)

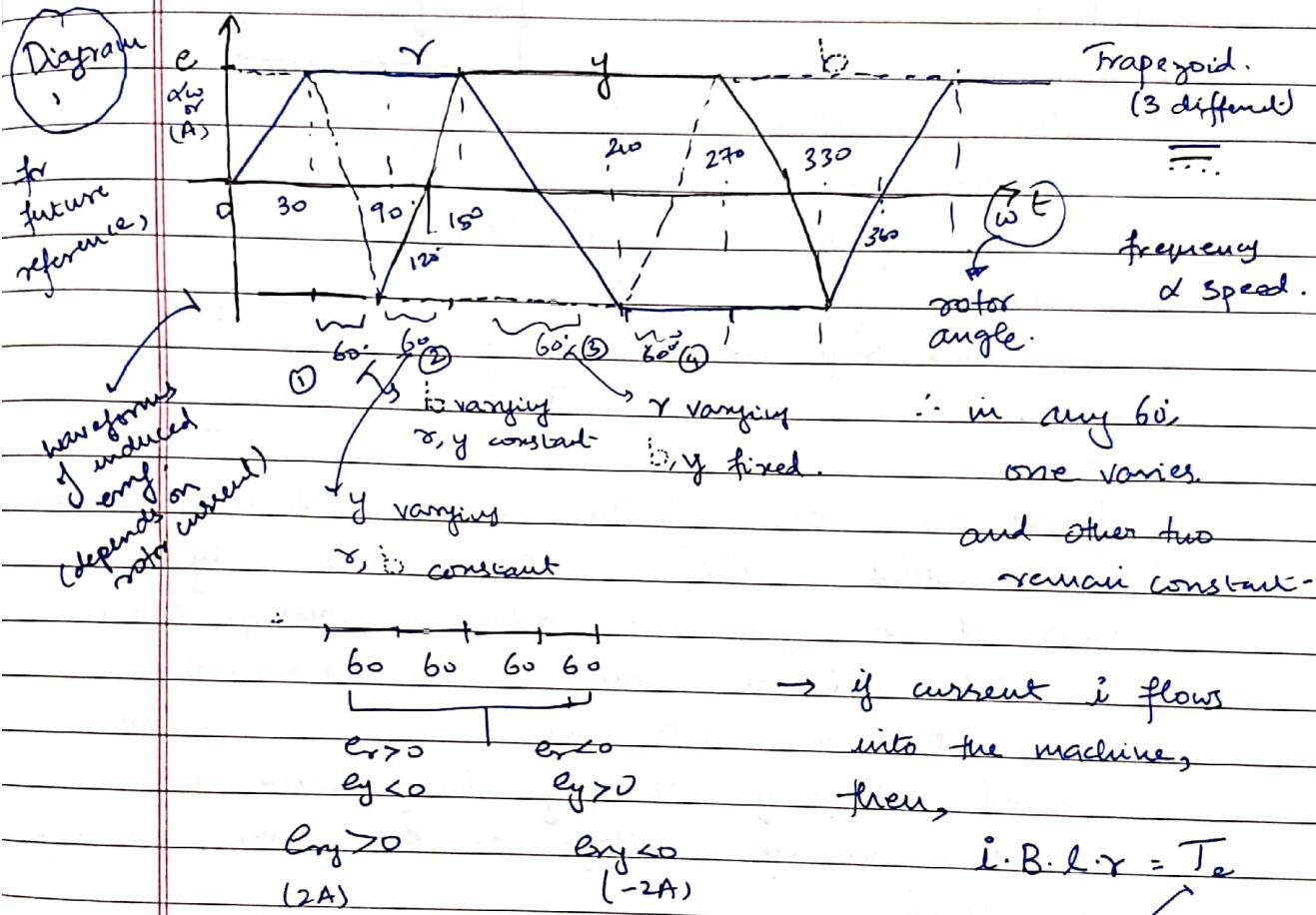

We want a fixed torque and not oscillating -  $(T_e)$

In the first 60° mentioned above,


① energize  $r, y$ , keep  $b$  open  
(what is fixed)      (what is fluctuating)

② energize  $r, b$ , keep  $y$  open

③ energize  $b, y$ , keep  $r$  open


④ energize  $r, y$ , keep  $b$  open

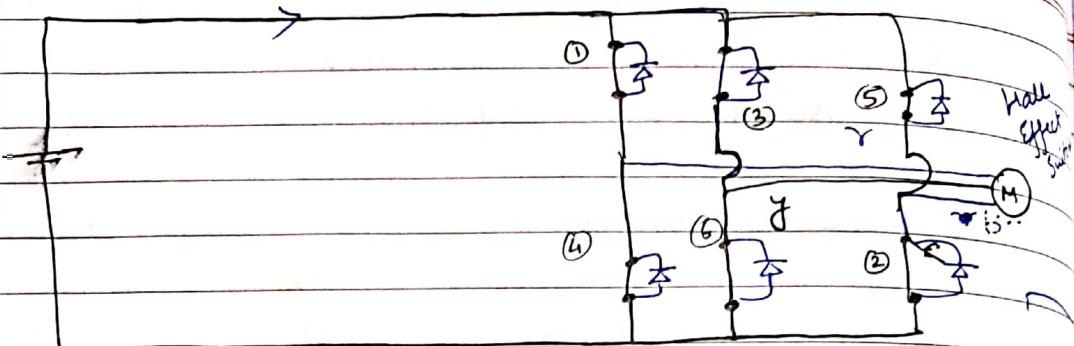but in the opposite sense of ①  
(check signs of  $e_{ry}$  in both cases)



Vary switches accordingly depending on the kind of output required

$\therefore$  In every  $60^\circ$ ,

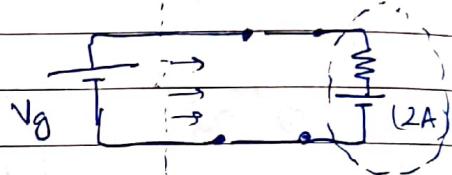

From the point of the source, at every interval it looks like a DC load only.

Now, if we feel like reducing voltage of the BLDC, switches must be operated within  $60^\circ$ , at some rate, by making them go on & off, thereby varying duty ratio, and so the average voltage on the motor, reducing its speed.


E.g.: In first  $60^\circ$ , switch (3) & (4).

For every  $60^\circ$  interval, one pair of switches are ON.

Once in  $60^\circ$ , one switch is turned off & another is turned ON.

Switches in each  $60^\circ$  interval can be operated high for PWM to control rotor voltage.


4/2/20

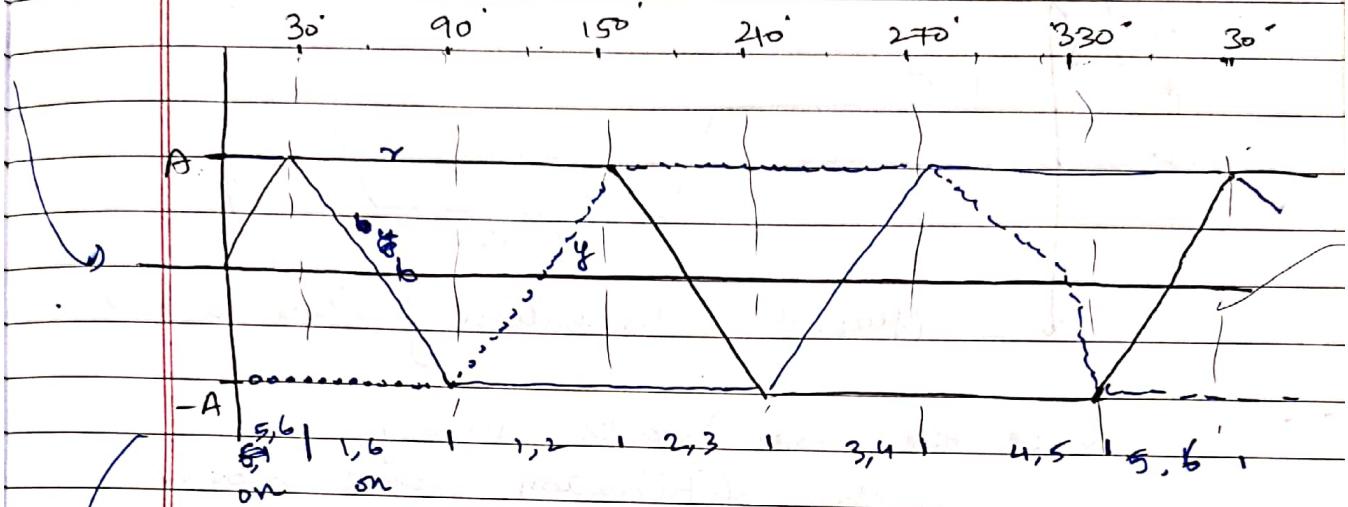

At a particular interval, if a phase is changing sign, don't use it.  
if it is steady, use that phase.


\* the patterns used is different from previous diagram. Please do not follow it.

Refer to 'x', 'y', 'b' notation used.

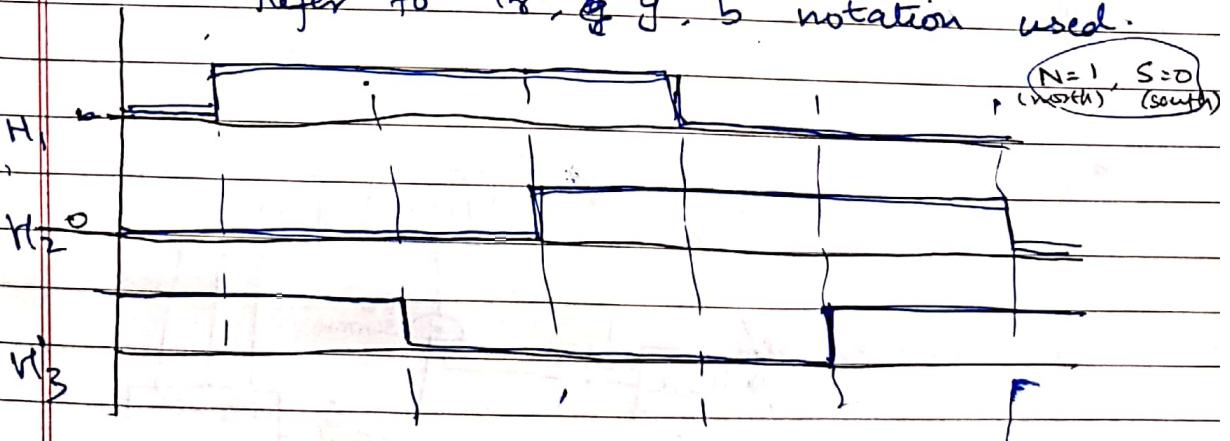

∴ now, writing algorithm for switches switching,  
Switch (1) :  $(H_1 \cdot \bar{H}_2)$ , when  $H_1$  is on &  $H_2$  is off.

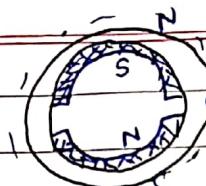Switch (2) :  $(H_1 \cdot \bar{H}_3)$  - boolean expression  
similarly, for all switches. logic gate.




observed  
from this  
point

both magnets are uniformly magnetized  
⇒ flux density is uniform


Magnetic field ⇒ flux

$B$  - flux density


$H$  - magnetic field intensity

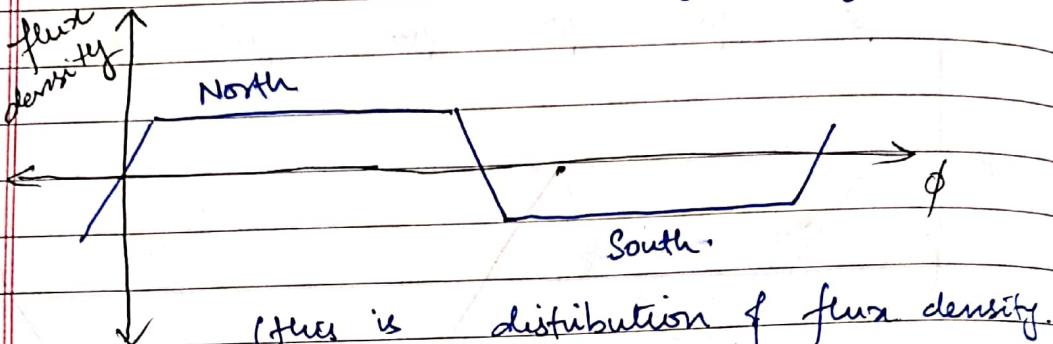

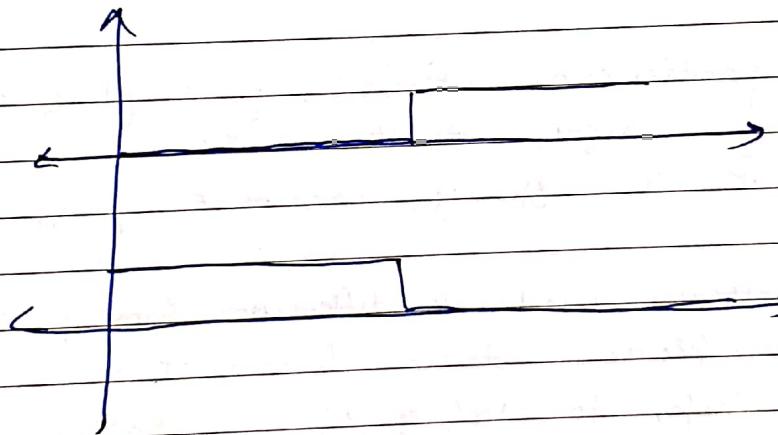Once the rotor starts moving,  
the distribution starts moving.




\*

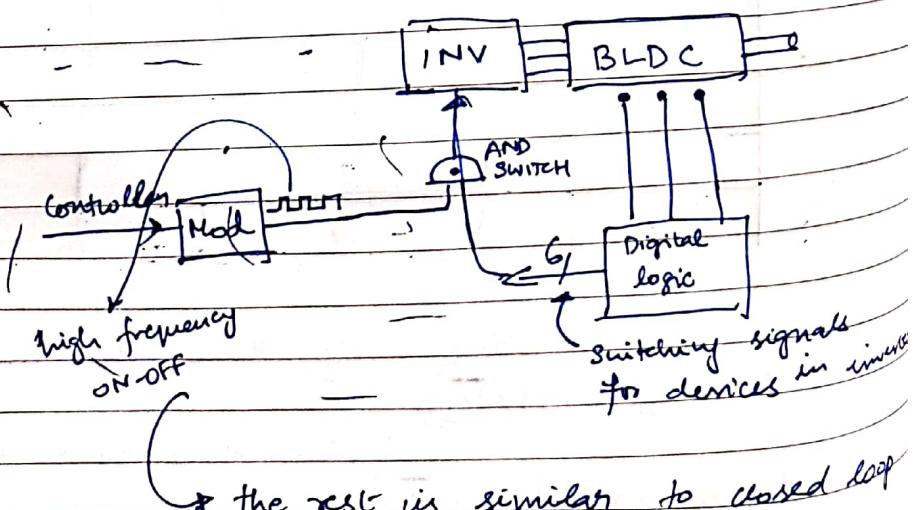

→ the rest is similar to closed loop structure seen before

Digital logic

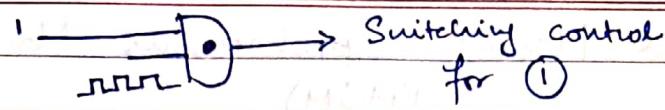


Switching control

for ①

These kinds of motors are used for, drones simple robotic devices unmanned vehicles.
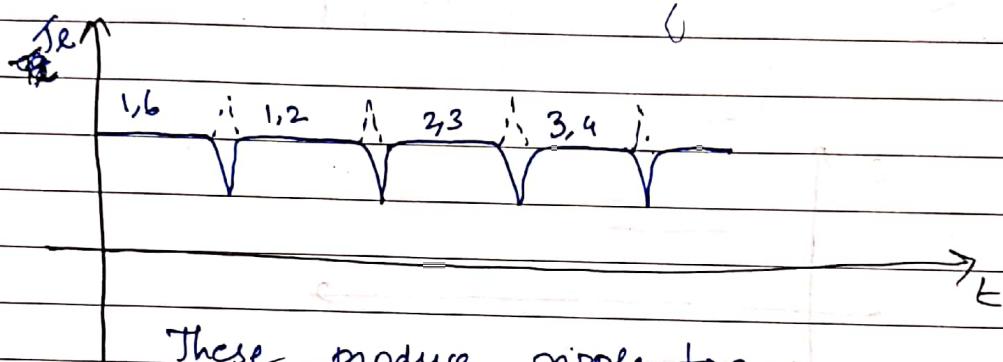
### Limitations:

\* During the 60° intervals rotor angle information is unavailable, we have the info only at the ends of the 60° intervals (when the switches switch).



These produce ripple torque  
(Because one phase goes out and new one comes in) which is unavoidable.

and the frequency depends on speed.


This ripple torque might result in the ~~change~~ compromise in the accuracy of the rotor angle.

∴ A low precision application would still be fine. Or if the rotating part has high moment of inertia, a dip in load torque won't be felt.

But for cases which requires higher precision, we use something else.

## Permanent Magnet Synchronous Machines (PMSM)

- Sinusoidal EMF

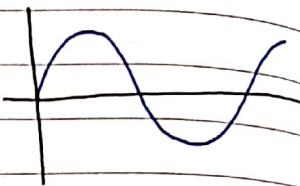

BLDC 1, 6 are ON

